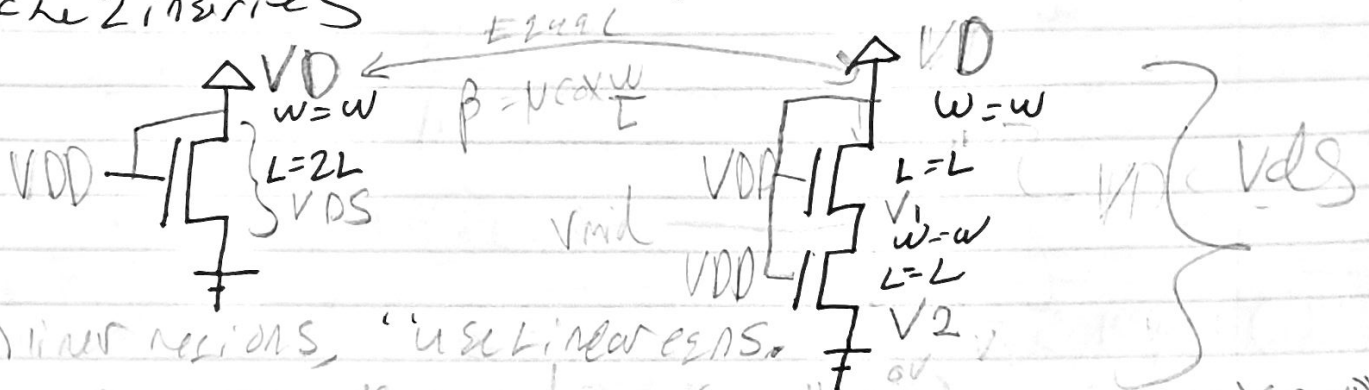


# Brian Landy

## Digital IC Design HW3

Lecture slides reviewed ✓

Show that current thru NMOS with  $L=2L$  is the same as 2 NMOS with length  $L$  connected in series.  $V_{DS}$  of longer transistor is same voltage as the middle of the 2 in series.



In linear regions, 'use linear eqns.

$$I = \beta (V_{GS} - V_t - \frac{V_{DS}}{2}) V_{DS} \quad I_1 = (\mu C_{ox} \frac{w}{L}) ((V_{DD} - V_t) - \frac{(V_{DD} - V_1)(V_{DD} - V_1)}{2})$$

$$\mu C_{ox} (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \quad I_2 = (\mu C_{ox} \frac{w}{L}) (V_{DD} - V_t - \frac{V_1}{2}) V_1$$

$$\frac{\mu}{2} C_{ox} (V_{GS} - V_t) (V_{DD} - V_t) - \frac{(V_{DD} - V_t)^2}{2} \quad V_{DS} = V_{DD} - 2V_t$$

$$= (V_{GS} - V_t)(V_{DD} - V_t) - \frac{(V_{DD} - V_t)^2}{2} \quad I_1 = I_2 \quad V_1 = V_{DD} - V_t$$

$$\frac{I_{DS} 2L}{\mu \mu C_{ox} 2} = \frac{I_1 L}{\mu \mu C_{ox} 2} + \frac{I_2 L}{\mu \mu C_{ox} 2}$$

$$2I_{DS}L = I_1L + I_2L$$

$$2I_{DS}L = I_{D1}L + I_{D2}L$$

$$2I_{DS}L = 2I_{DS}L$$

$$I_{DS} = I_{DS} \checkmark$$

3  $L = 14 \mu m \rightarrow 14 \times 10^{-6} m$   $\epsilon_0 \times 4.5$   $\frac{1}{\epsilon_0} = 10^{12} \rightarrow 10 \times 10^{-10}$

$C_g = \epsilon_0 \times W \cdot L \cdot \frac{1}{t_{ox}}$

$C_g = 4.5 \cdot W \cdot 14 \times 10^{-9} \cdot \frac{1}{10 \times 10^{-10}}$

$\frac{C_g}{W} = \frac{4.5 \cdot 14 \times 10^{-9}}{10 \times 10^{-10}} = 63$

$\frac{C_g}{W} = \frac{63 F}{M \times 10^{-6}} = \frac{63 \times 10^{-6}}{1 \mu m}$

$C_g$  increases by  $63 \times 10^{-6} F$  per micron

4) PMOS  $V_t = 0.3V$ . Lower  $V_t$  by magnitude of  $100 mV$ .  $V_{DS} = V_{GS} = V_{dd} = 1V$ , how much will current change? (in saturation) How about power? Relation between speed + power?

$I_{DSS} + I_{DS} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{GS} - |V_t|)^2$

$V_{DS} = 1 - 0.3 = 0.7$

$I_{DSS} @ V_t = 0.3V \rightarrow \frac{1}{2} K_p (1 - 0.3)^2$

$I_{DS} = 0.245 K_p A_{res} |_{power} = 0.7 \cdot 0.245 K_p = 0.1715 K_p \text{ Watts}$


$I_{DSS} @ V_t = 0.2V$

$I_{DS} = \frac{1}{2} K_p (1 - 0.2)^2$

$I_{DS} = 0.32 K_p |_{power} = 0.8 \cdot 0.32 K_p = 0.256 K_p \text{ Watts}$

For a voltage change of  $100 mV$ , power changes by a lot more. Speeding the circuit up will require more and more power to keep in CMOS. It's not linear.

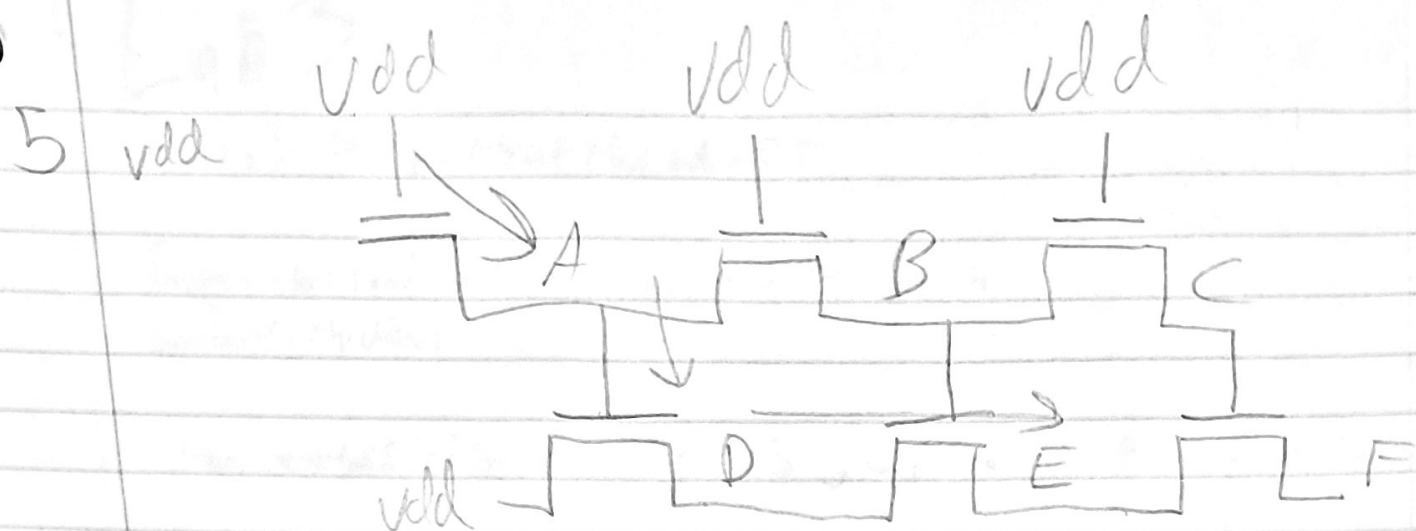$100 mV$  is at a cost of  $0.0845 K_p \text{ Watts}$



$$A: V_{DD} - V_{tn}$$

$$B: V_{DD} - 2V_{tn}$$

$$C: V_{DD} - 3V_{tn}$$

$$D: V_{DD} - 2V_{tn}$$

$$E: V_{DD} - 3V_{tn}$$

$$F: V_{DD} - 4V_{tn}$$